

# How do Ignition Coils Work?

Read

<http://www.linnbenton.edu/auto/perform/ignition.html>

and

[http://www.linnbenton.edu/auto/perform/how\\_spark.html](http://www.linnbenton.edu/auto/perform/how_spark.html)

View animation at

[http://gillinstruments.com/products/digital\\_ignition/introduction/graphics/ignition\\_coil.swf](http://gillinstruments.com/products/digital_ignition/introduction/graphics/ignition_coil.swf)

(above link works in Chrome and Firefox. May not work in Explorer)


# What happens if the coil wire is unplugged?

Any open circuit in the secondary spark plug current path will create a VERY high voltage in the secondary coil.

This can short out (burn through) the secondary winding insulation causing the coil to work at reduced power (misfire under load)

It is possible for high voltage to burn through insulation of primary windings causing a voltage spike to burn out the Power Transistor

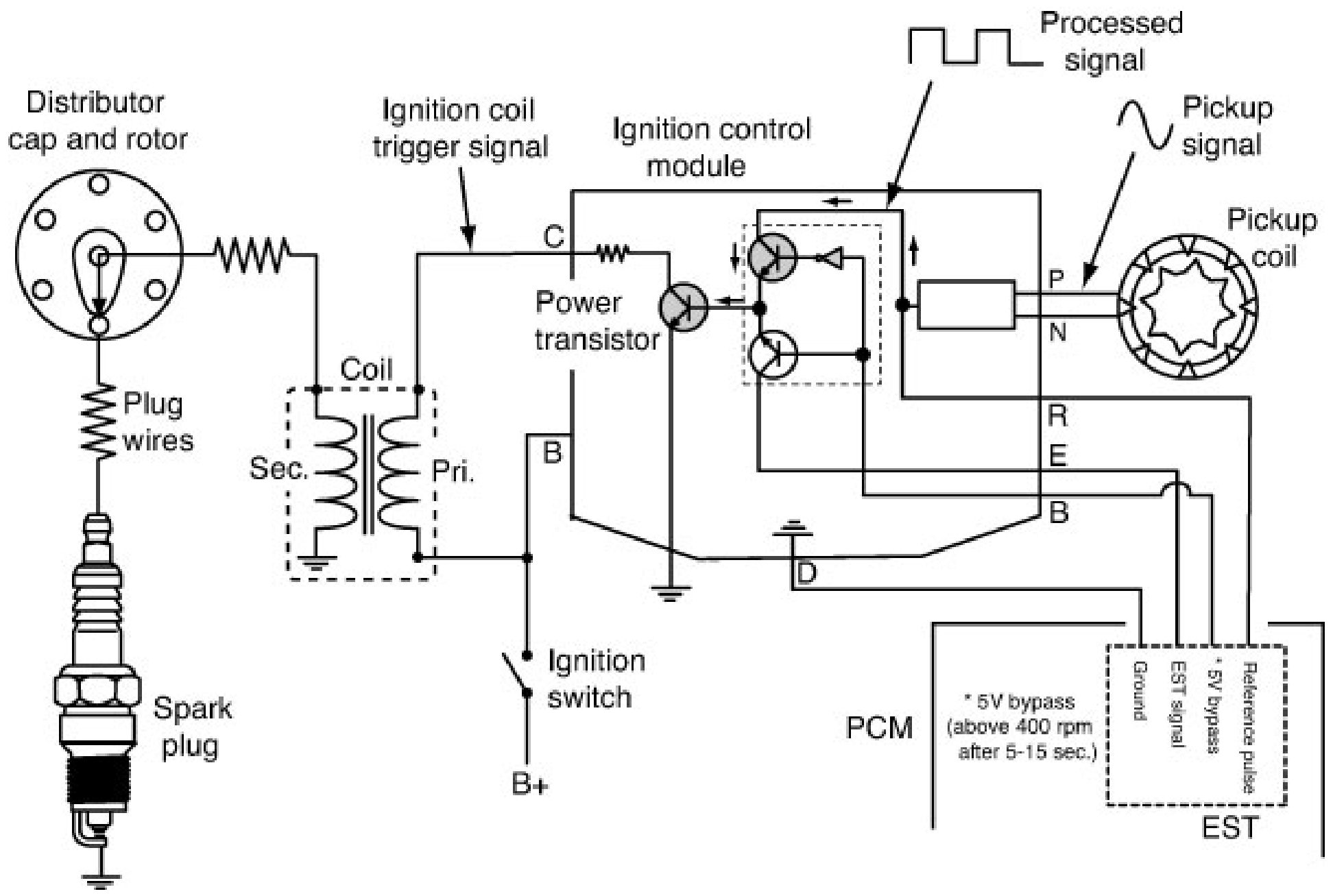If this happens the vehicle will not run until the ignition control module is replaced.



Distributor cap and rotor


Ignition coil trigger signal

Ignition control module


Processed signal

Pickup signal



Pickup coil

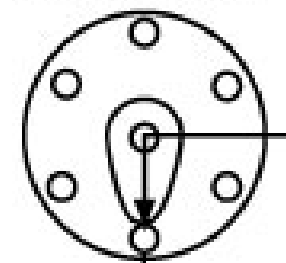

Plug wires

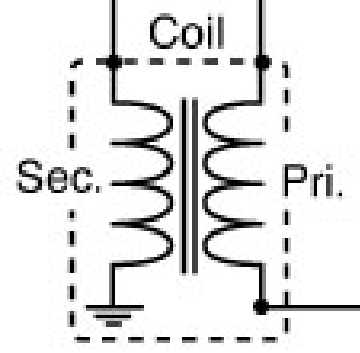

Power transistor

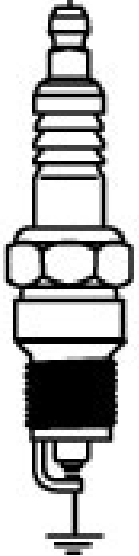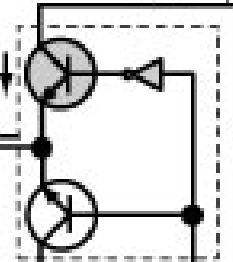

Spark plug

Ignition switch

PCM

\* 5V bypass (above 400 rpm after 5-15 sec.)



EST

B+

D

B

C

P

N

R

E

B


Always use Extreme Care when cranking engine with any spark plug wire removed!

You will do this when compression testing.

You can easily damage or destroy an ignition coil and/or ignition control module if the coil makes spark when there is an open circuit.
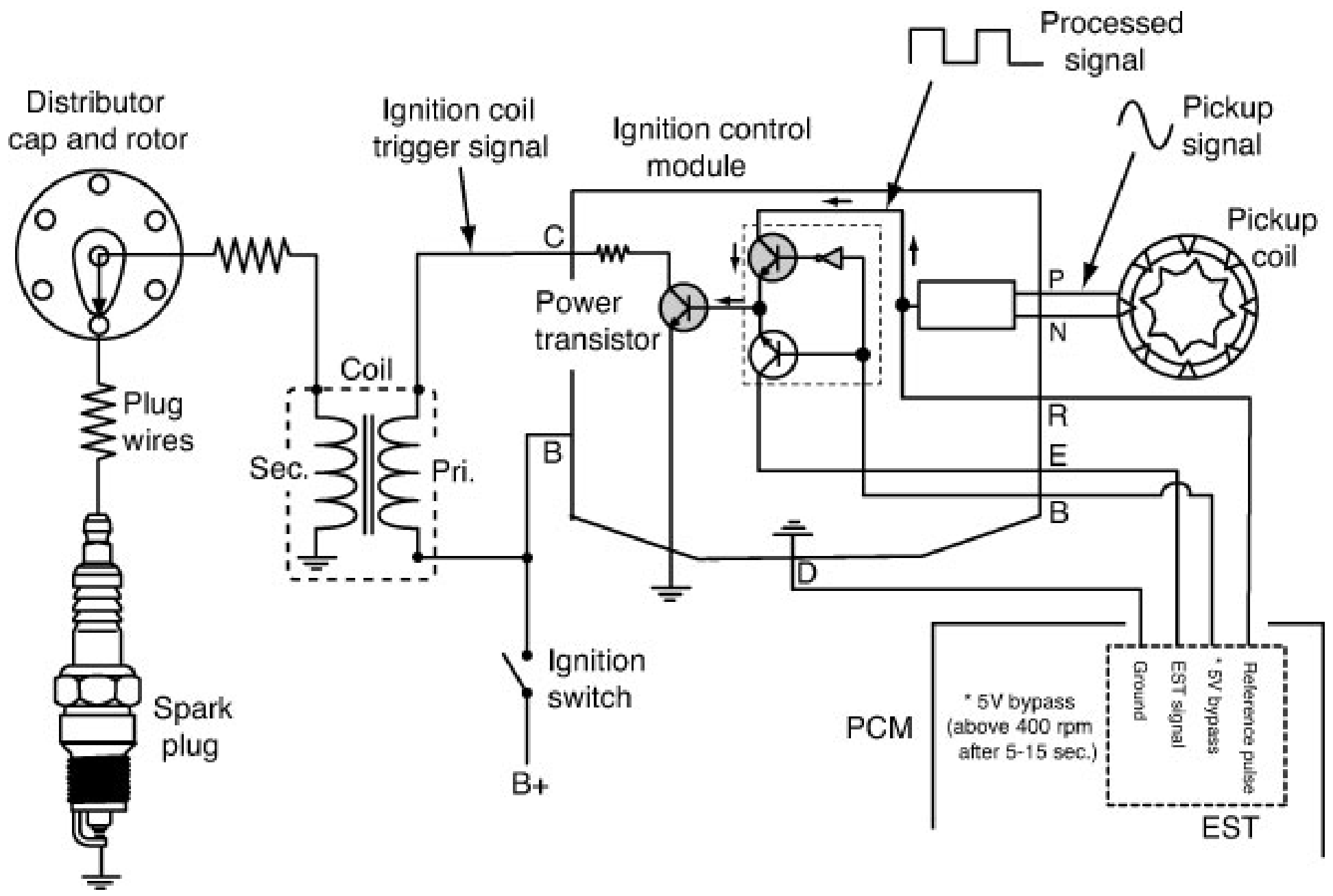
# What if you have No Spark?

- Figure out where the problem is!
- Cut the system in half to eliminate components.
- The ignition coil is best place to decide if the problem is in the primary or secondary




# How do you check the Primary?

A 12 volt test light connected to battery Positive and coil Negative will Flash ON/OFF while cranking.

No ON-OFF at test light means either no positive voltage to the coil, or the coil is not being turned ON and OFF at the power transistor

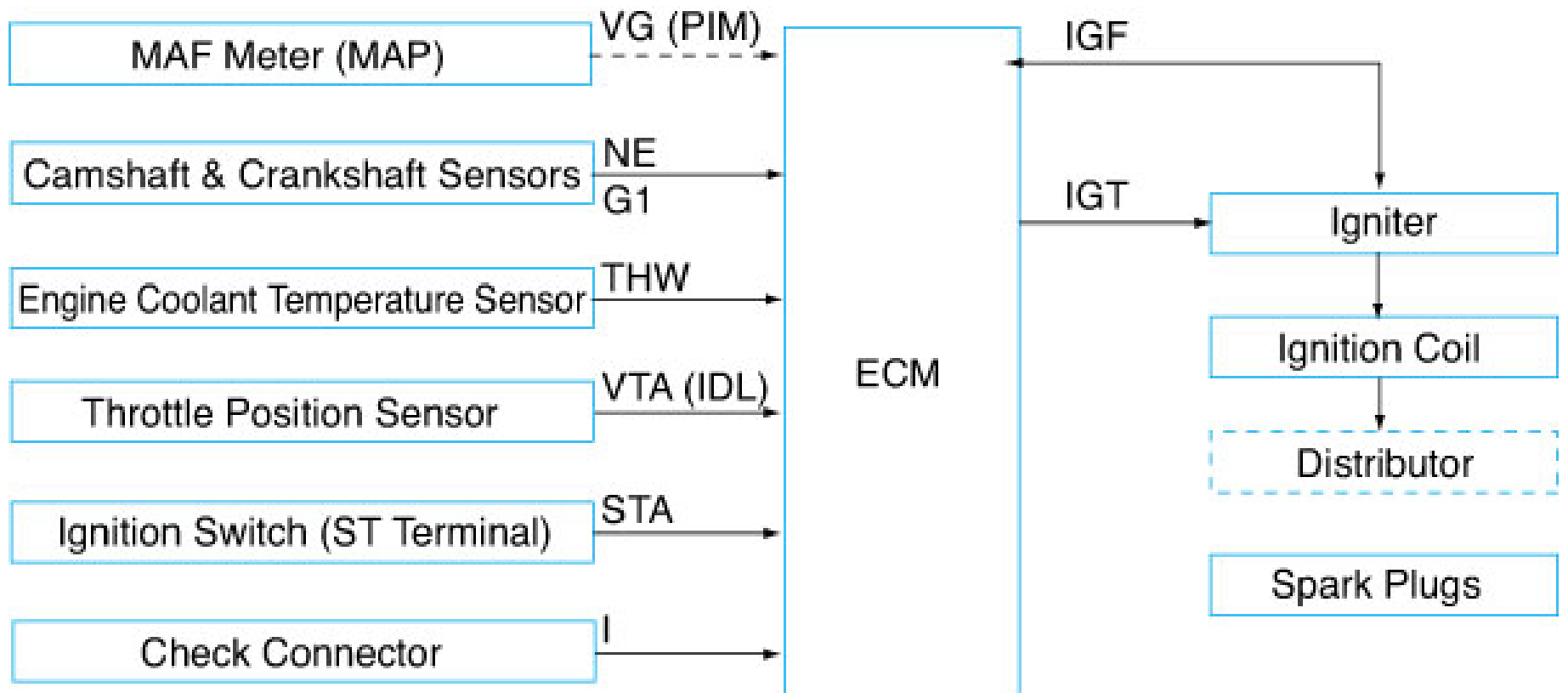- If the coil has Positive voltage but is not being switched ON/OFF check the sensors that trigger the Ignition control module.
- Scan tool is best to see if crank, or cam signals are being received.
- Systems use different controls, use service information for diagnosis





Ignition Systems

# How do you check the Secondary?

Use an Ohm Meter to check coil winding resistance.

Open circuit means – bad coil

Slightly low resistance (check specifications) indicate a shorted coil.

Coils that measure proper ohm readings may not be good coils as insulation may hold for Ohm test but fail at high voltage

# How do you check the Secondary?


Do not neglect to test coil and plug wires with ohm meter

Do a thorough visual inspection to look for any carbon tracks or indication that the insulation has failed

What are the basic types of ignition systems?
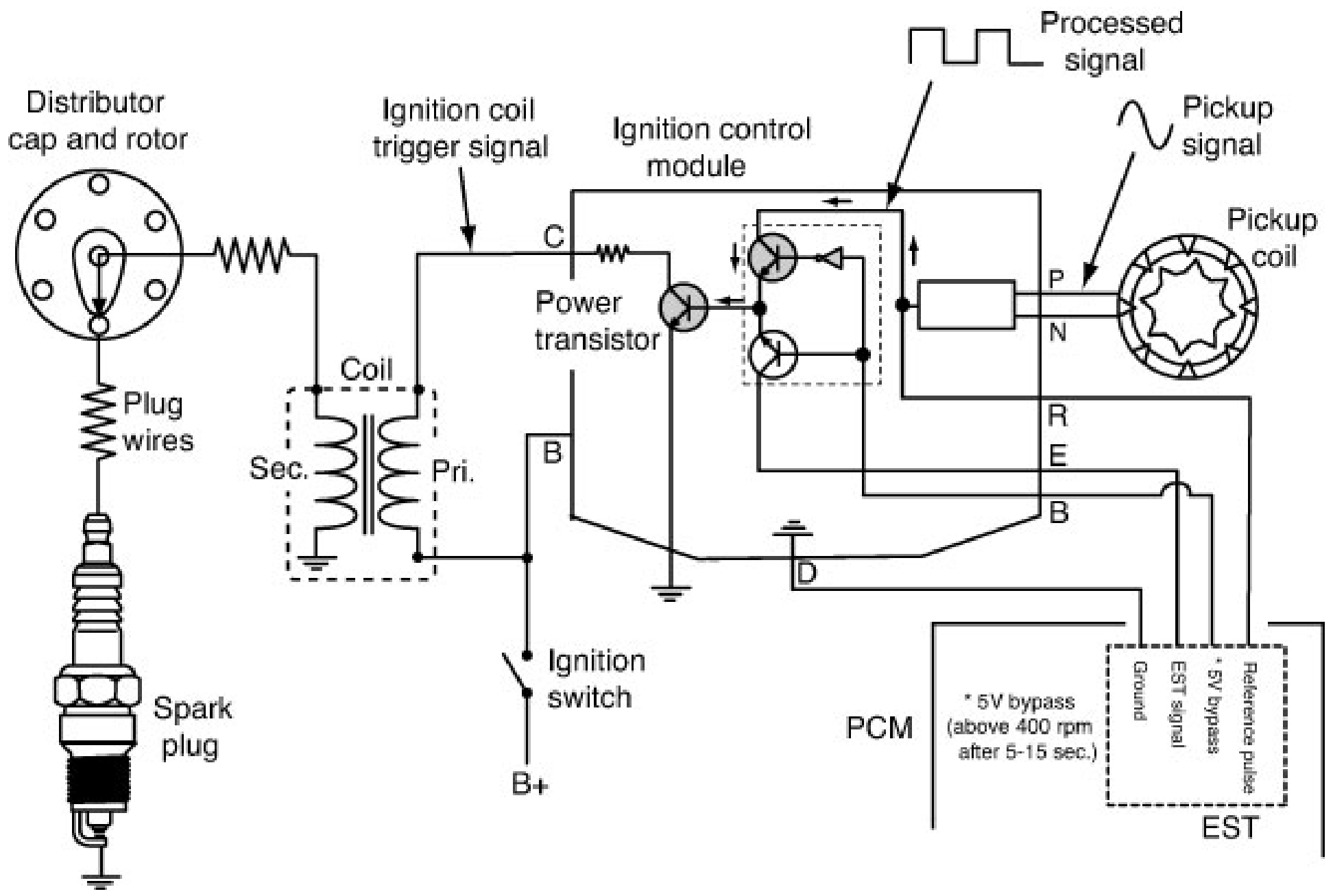
## Distributor Ignition (DI)

Will use one coil with a distributor cap and rotor to send spark to each cylinder



Distributor cap and rotor

Ignition coil trigger signal

Ignition control module

Processed signal

Pickup signal

Pickup coil

Plug wires

Coil  
Sec.  
Pri.

Power transistor

Spark plug

Ignition switch

PCM

\* 5V bypass (above 400 rpm after 5-15 sec.)

Reference pulse  
EST signal  
Ground

EST

B+

D

B

C

P

N

R

E

B

# What are the basic types of ignition systems?


Distributor Ignition (DI)


Distributor Less Ignition System (DIS)  
also called Electronic Ignition (EI)  
and Wasted Spark Ignition

Will use one coil for every pair of cylinders.

Fires spark plug on compression AND exhaust stroke

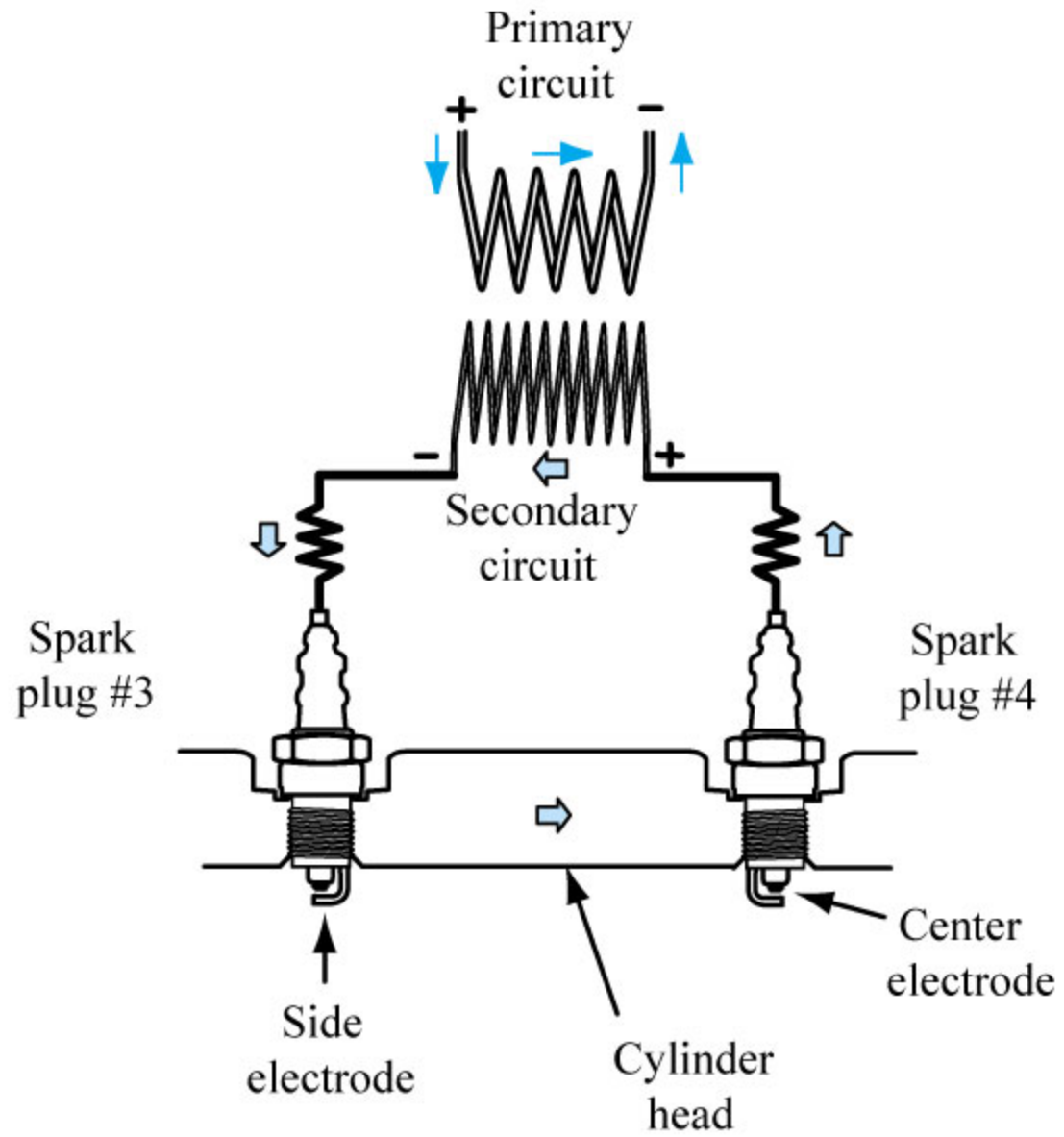When it fires on exhaust the spark is “Wasted”



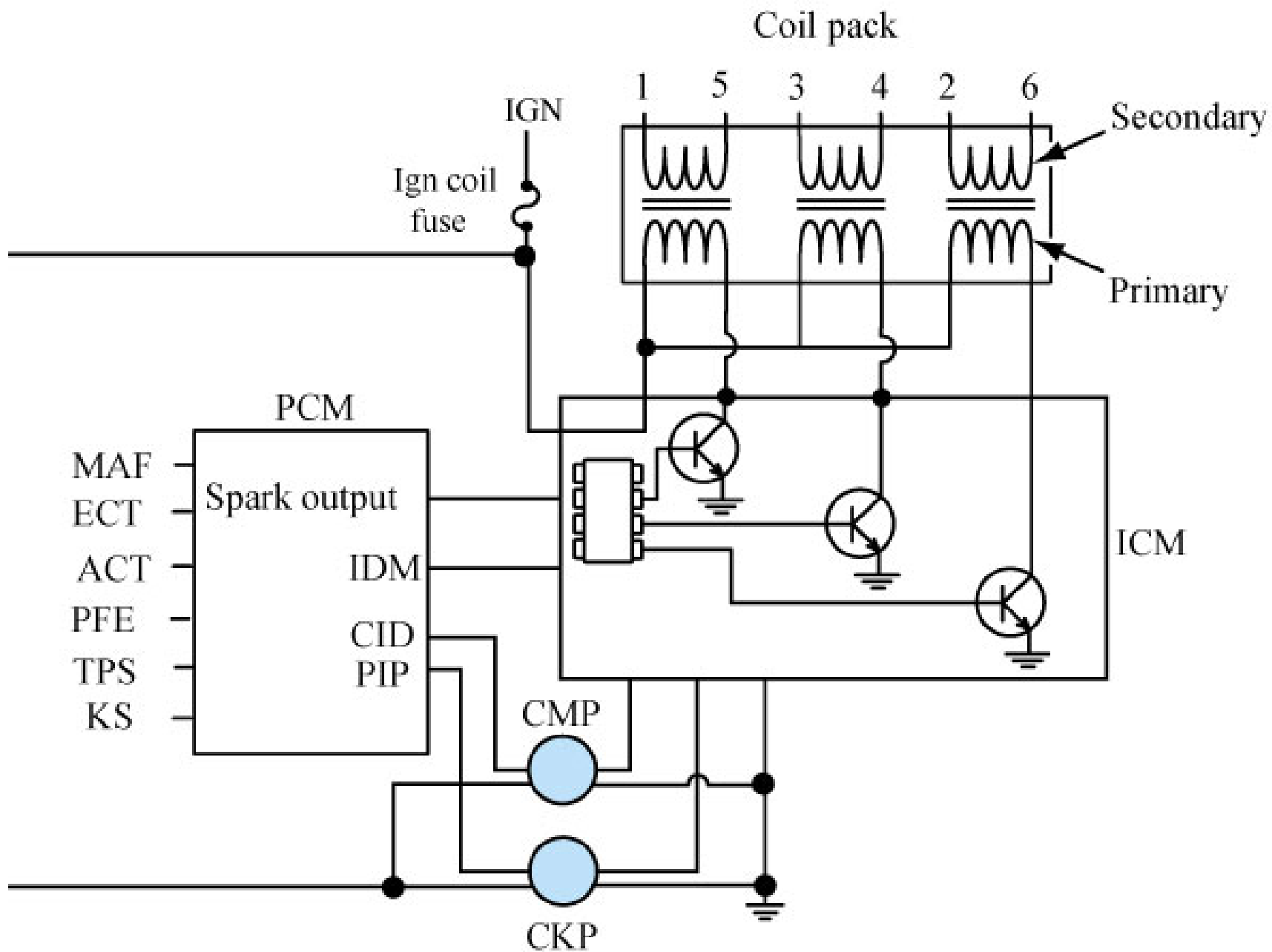



# What are the basic types of ignition systems?

Distributor Ignition (DI)

Wasted Spark Ignition (EI)


Distributor Less Ignition System (DIS)

also called Electronic Ignition (EI)

And Coil On Plug

Or Coil Near Plug

Will use one coil for each cylinders.

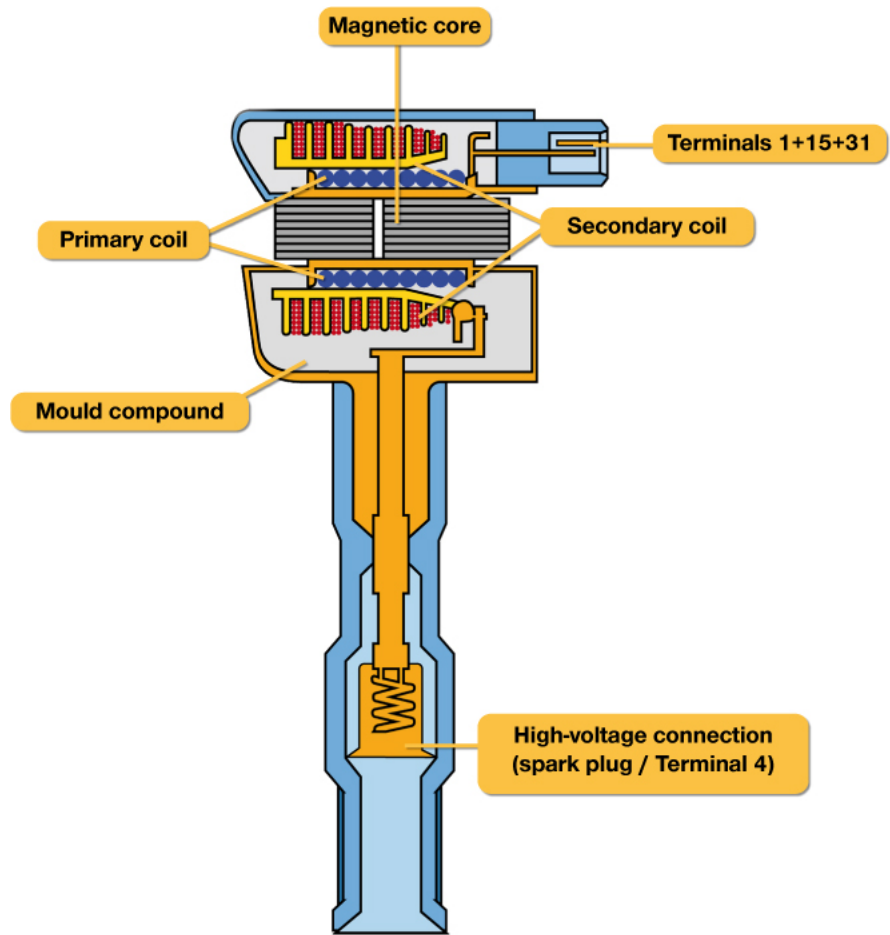

# What are the basic types of ignition systems?

**Distributor Ignition (DI)**  
**Wasted Spark Ignition (EI)**  
**Coil On Plug (EI)**  
**Coil Near Plug (EI)**

A good article that explains these types of ignition

<http://leakylugnut.com/electronics/ignition-systems/>